ELTK1100 FORMULAS

Ohm's Law

$$I = \frac{V_T}{R}$$

Voltage Drop

$$V_x = I_x * R_x$$

Series circuits (sub-circuits)

$$I_T = I_1 = I_2 = I_3 = \dots$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = \frac{V_T}{R_T}$$

KVL

$$V_T = V_1 + V_2 + V_3 + \dots$$

Voltage Division (for series resistors)

$$V_x = \frac{R_x}{R_T} * V_T$$

Current

$$I = \frac{q}{t}$$

$$1 C = 6.25 * 10^{18} electrons$$

Power

$$P = V_T I = I^2 R = \frac{{V_T}^2}{R}$$

1 hp = 746 W

Energy

Energy =
$$P t$$

Cost = Energy * $\frac{cost}{kW \cdot h}$

P in kW t in h Energy in kW•h

Heat

$$Q = M C \Delta T \qquad \Delta T = T_2 - T_1$$
Efficiency = $\frac{Q}{Heat \ Produced} * 100\%$
Heat $Produced = \frac{P \ t}{4.187}$

$$P \ in \ W \ t \ in \ s$$

Parallel circuits (sub-circuits)

$$I_{T} = I_{1} = I_{2} = I_{3} = \dots$$

$$R_{T} = R_{1} + R_{2} + R_{3} + \dots$$

$$I_{T} = \frac{V_{T}}{R}$$

$$V_{T} = V_{1} = V_{2} = V_{3} = \dots$$

$$\frac{1}{R_{T}} = \frac{1}{R_{1}} + \frac{1}{R_{2}} + \frac{1}{R_{3}} + \dots$$

$$I_{T} = \frac{V_{T}}{R_{T}}$$

KCL

$$I_T = I_1 + I_2 + I_3 + \dots$$

Current Division (for parallel resistors)

$$I_{x} = \frac{R_{eq}}{R_{x}} * I_{T}$$

Current Division (for 2 parallel resistors)

$$I_x = \frac{Opposite}{Sum} * I_T$$

Two resistors in parallel

$$R_1 \parallel R_2 = \frac{R_1 * R_2}{(R_1 + R_2)}$$

n equal resistors in parallel

$$R_T = \frac{R}{n}$$

Conductance

$$G = \frac{1}{R}$$

 $G_T = G_1 + G_2 + G_3 +$
 $I_T = V_T G_T$

Conductor Resistance

$$R = \frac{\rho \ell}{A}$$

Metric

1
$$mil = 0.001''$$

$$A = \frac{\pi d^2}{4} \qquad A = d^2$$

$$A = d^{2}$$

$$1 CM = 1 mil^2$$

Effect of Temperature on Resistance

$$R_{T_2} = \frac{\left(1 + \alpha_0 T_2\right)}{\left(1 + \alpha_0 T_1\right)} * R_{T_1}$$

$$R_T = (1 + \alpha_0 T) * R_0$$

Magnetomotive Force

$$F_M = NI$$

Magnetic Flux

$$\Phi = \frac{F_M}{R_M}$$

Dynamic Induction

$$V_{IND} = N B \ell v$$

Static Induction

$$V_{IND} = N \frac{\Delta \Phi}{\Delta t} \qquad \Delta \Phi = \Phi_1 - \Phi_2$$

Error

% Error =
$$\left| \frac{Actual - Measured}{Actual} \right| * 100%$$

Battery Capacity

Capacity = Discharge Rate * time

Inductance

$$L = \frac{N^2}{R_M}$$

$$V_{IND} = L \frac{\Delta I}{\Delta t}$$

$$\Delta I = I_1 - I_2$$
Series $L_T = L_1 + L_2 + L_3 + \dots$

Parallel
$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$$

Batteries

Series
$$E_T = S E$$
 $r_T = S r$

Parallel $E_T = E$ $r_T = \frac{r}{P}$

Series/Parallel $E_T = S E$ $r_T = \frac{S r}{P}$

$$V_T = E_T - I_T r_T$$